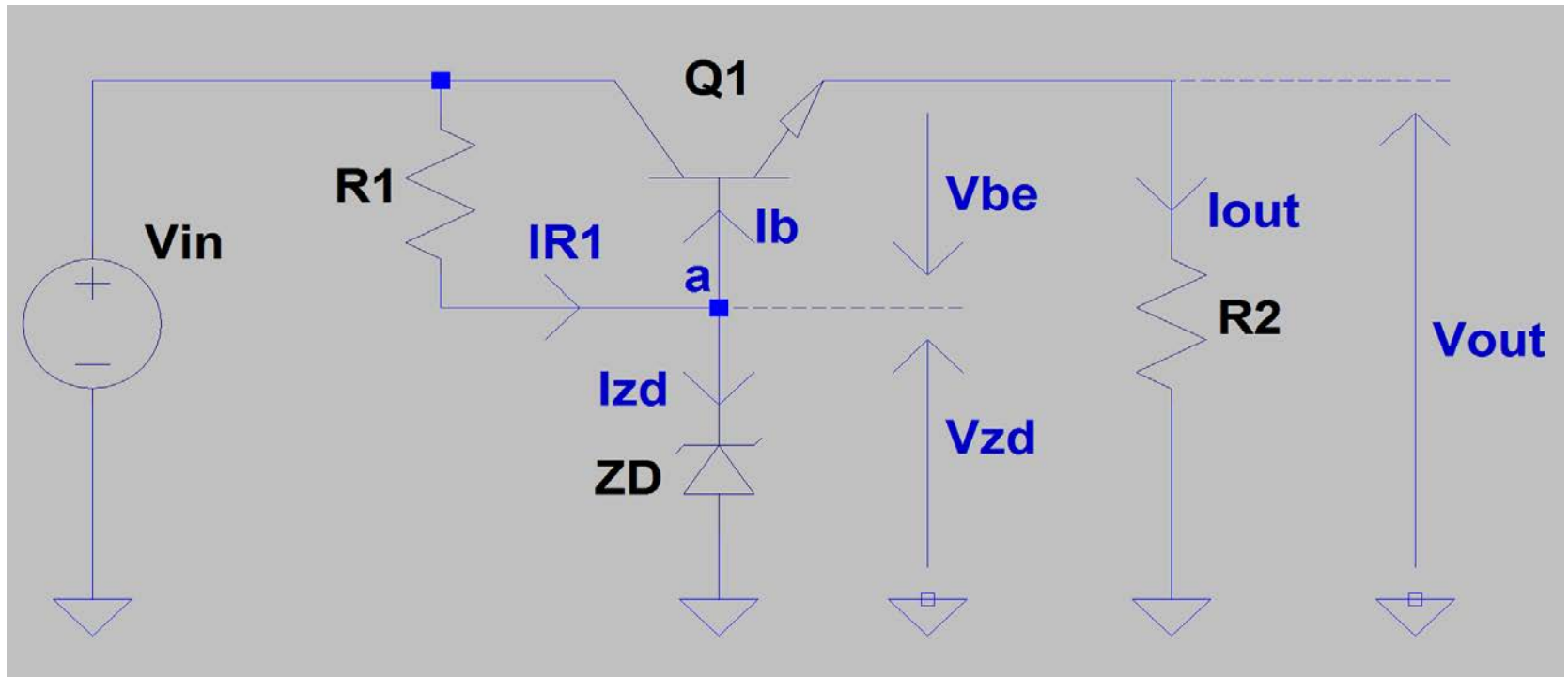


# Stabilizatori napona sa bipolarnim tranzistorima



$$V_{out} = V_{zd} - V_{be}$$

$$I_{R1} = \frac{V_{in} - V_{zd}}{R_1} = I_{zd} + I_b$$

$$R_1 \leq \frac{V_{in\_min} - V_{zd}}{I_{out\_max} / h_{FE\_min} + I_{zd\_min}}$$

# Primer 1

- Projektovati stabilizator napona sa tranzistorom za izlazni napon 5V i potrošač čija se struja menja od 0,1 do 1A, ukoliko je poznato da se ulazni napon menja u granicama od 8 do 10V.
- Prvo je neophodno odrediti napon zenerove diode:
- $V_{zd} = V_{out} + V_{be} = 5V + 0,6V = 5,6V$

# Izbor tranzistora


- Nakon toga potrebno je odrediti maksimalnu snagu disipacija na tranzistoru kako bi se odabrao odgovarajući model tranzistora
- $P_{d\_max} = (V_{in\_max} - V_{out}) \cdot I_{out\_max} = (10V - 5V) \cdot 1A = 5W$
- Dakle potreban nam je tranzistor sa sledećim parametrima:  $V_{br} > 10V$ ,  $I_{c\_max} > 1A$ ,  $P_{d\_max} > 5W$  i  $h_{FE} > 100$ .
- Tranzistor koji zadovoljava ove uslove je na primer 2SCR574D:  $V_{br} = V_{CEO} = 80V$ ,  $I_{c\_max} = 2A$ ,  $P_{d\_max} = 10W$  i  $h_{FE} = 120$  do 390.

# Proračuni komponenti

- $R_1 \leq \frac{V_{in\_min} - V_{zd}}{I_{out\_max}/h_{FE\_min} + I_{zd\_min}} = \frac{8V - 5,6V}{1A/120 + 5mA} = 180\Omega$

- $P_{zd\_max} = V_{zd} \cdot \left( \frac{V_{in\_max} - V_{zd}}{R_1} - \frac{I_{out\_min}}{h_{FE\_max}} \right) =$   
 $= 5,6V \cdot \left( \frac{10V - 5,6V}{180\Omega} - \frac{0,1A}{390} \right) = 0,135W$

# Prekostrujna zaštita

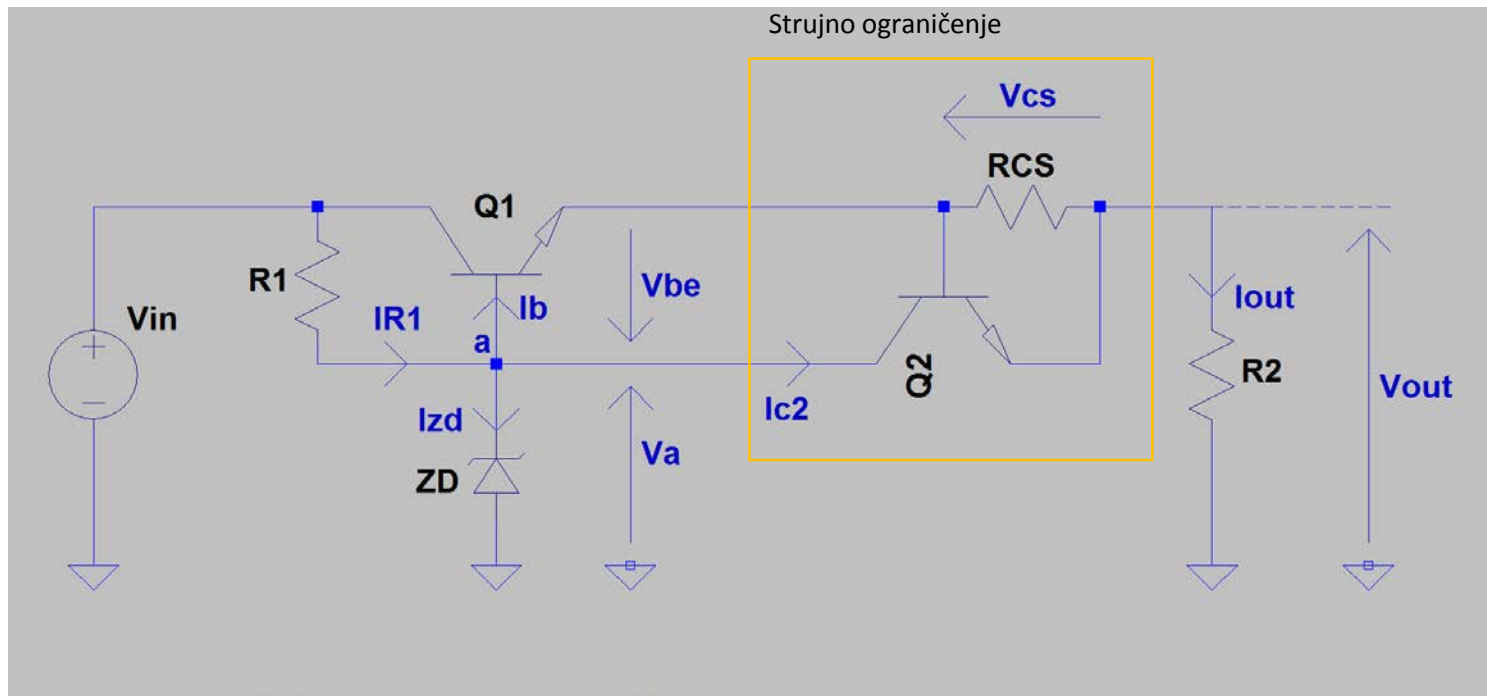

$$I_{R1} = I_b + I_{zd} + I_{c2}$$

$$I_{out\_CL} = 1,1 \cdot I_{out\_max}$$

$$R_{CS} = \frac{V_{be}}{I_{out\_CL}}$$


# Dejstvo strujnog ograničenja

- Pri dostizanju vrednosti strujnog ograničenja za napon na čvoru  $a$   $V_a$  važi sledeća jednakost:
- $V_a = R_2 \cdot I_{out_{CL}} + V_{CS} + V_{be} = R_2 \cdot I_{out_{CL}} + 1,2V = V_{zd}$
- za  $R_2 \leq \frac{V_{zd} - 1,2V}{I_{out_{CL}}}$  zener dioda izlazi iz proboja
- Za  $R_2 = 0$ , snaga disipacije na  $Q_1$  je maksimalna i data je izrazom:
- $P_{dmax} = I_{out_{CL}} \cdot (V_{in_{max}} - V_{CS}) = I_{out_{CL}} \cdot (V_{in_{max}} - 0,6V)$

# Tranzistor Q2

- $V_{ce2\_max} = V_{CS} + V_{be} = 1,2V$
- $I_{c2\_max} = \frac{V_{in\_max} - V_{be} - V_{CS}}{R_1} - \frac{I_{out\_CL}}{h_{FE\_max}}$
- $P_{d2\_max} = V_{ce2\_max} \cdot I_{c2\_max}$
- Nedostatak koje ima opisano kolo je povećanje izlazne otpornosti uvođenjem otpornika  $R_{CS}$ .
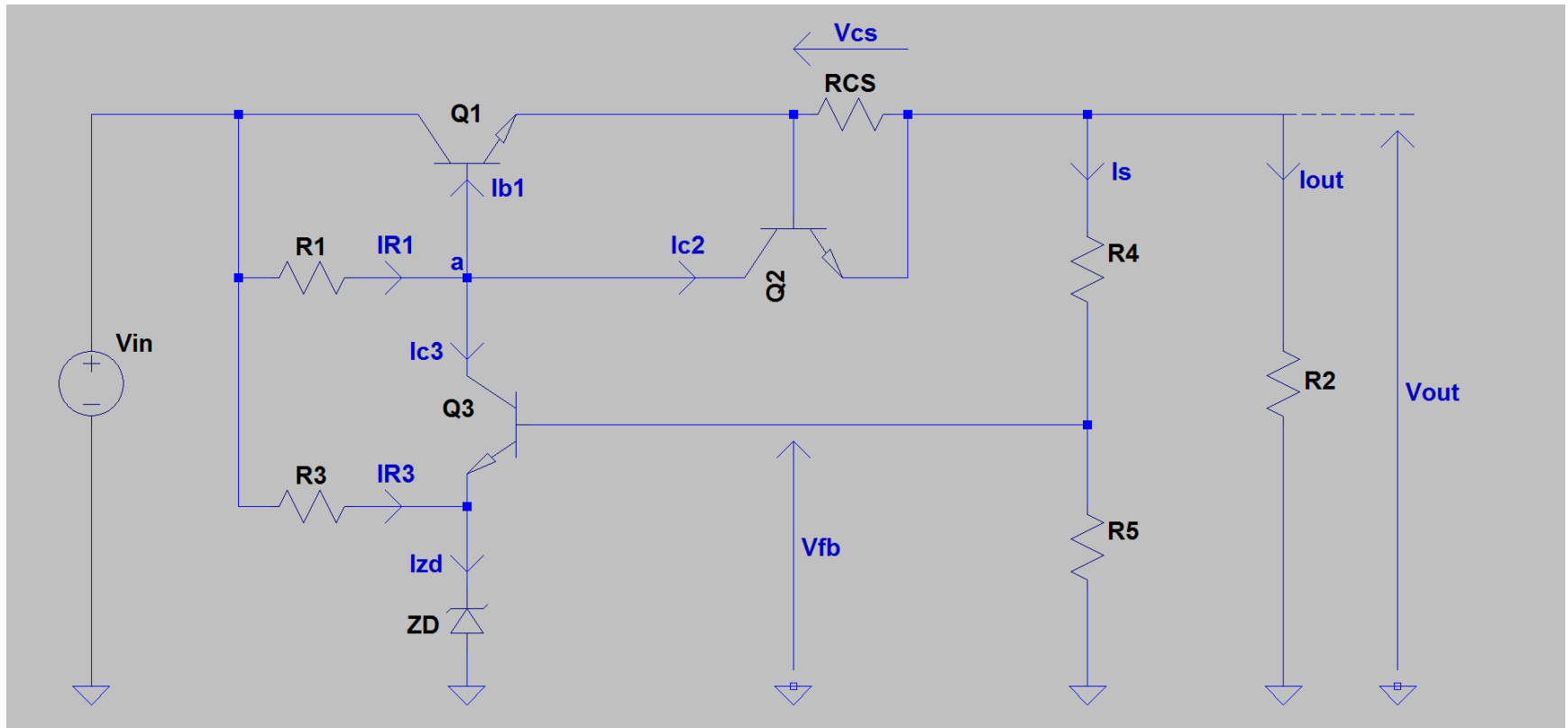
# Prekostrujna zaštita i naponskom povratnom spregom sa izlaza






# Proračun komponenti



- Za  $I_{R_4-R_5} \gg I_{b3}$  razdelnik možemo smatrati idealnim
- $V_{fb} = \frac{R_5}{R_4+R_5} \cdot V_{out} = V_{zd} + V_{be3}$   
$$\Rightarrow V_{out} = \left(1 + \frac{R_4}{R_5}\right) \cdot (V_{zd} + V_{be3})$$
- $R_1$  obezbeđuje baznu struju tranzistora  $Q_1$
- $R_1 < \frac{V_{in\_min} - V_{out} - V_{CS\_max} - V_{be1}}{(I_{out\_CL} + I_s) / h_{FE\_min}}$
- $R_3$  obezbeđuje potrebnu struju da bi zener dioda sigurno bila u probou
- $R_3 \leq \frac{V_{in\_min} - V_{zd}}{I_{zd\_min}}$

# Strujni izvori – strujni regulatori

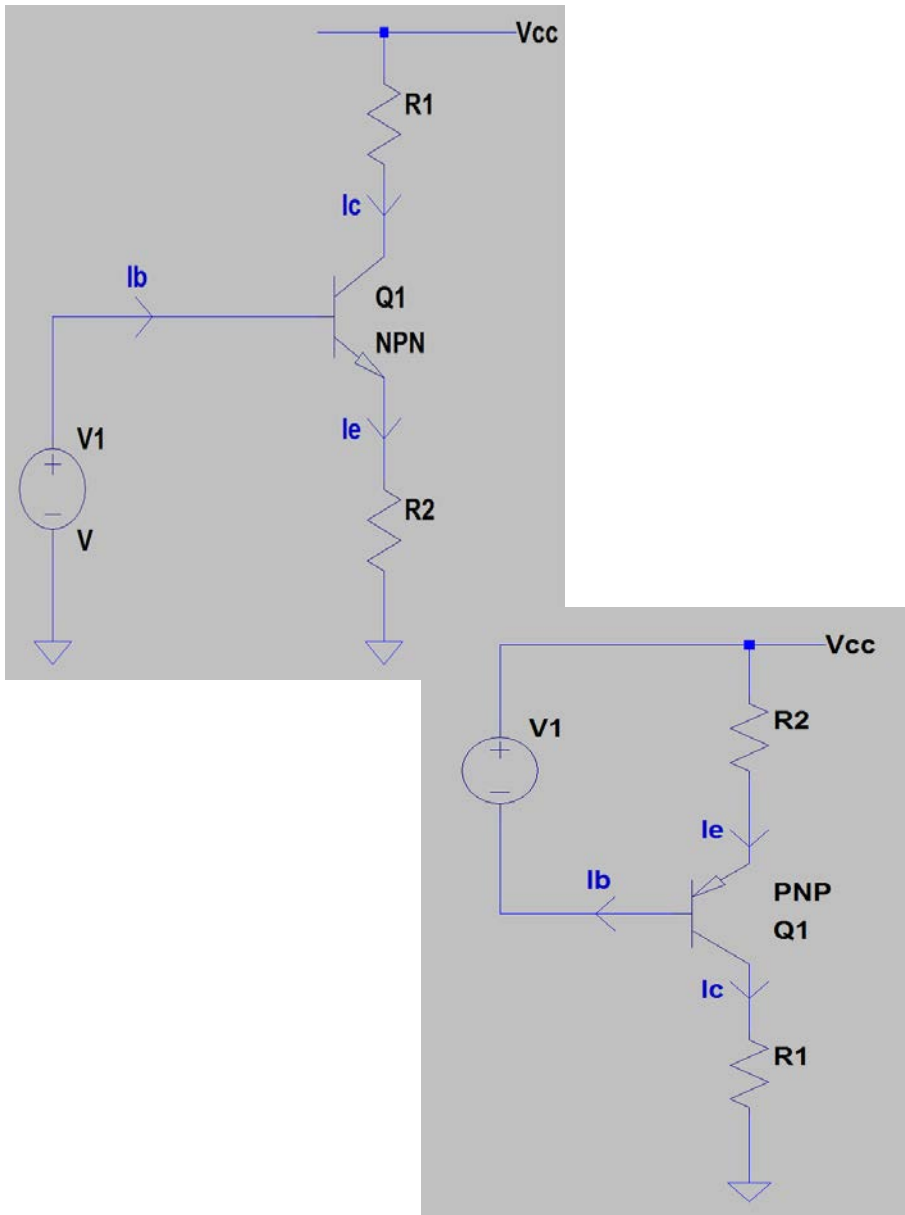


- $V_1 = V_{be} + I_e \cdot R_2$
- $I_e = \frac{V_1 - V_{be}}{R_2} = \text{const}$
- Za veliko  $h_{FE}$
- $I_c = I_e$
- $V_{cc} - R_1 \cdot I_c - V_{ce} - R_2 \cdot I_e = 0$
- $0 \leq R_1 < \left( \frac{V_{cc} - V_{ce\_sat}}{I_c} - R_2 \right)$

# Realizacija

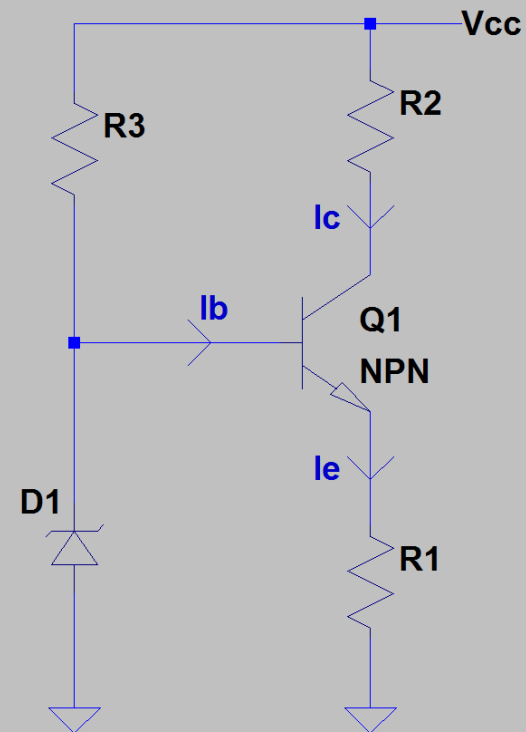
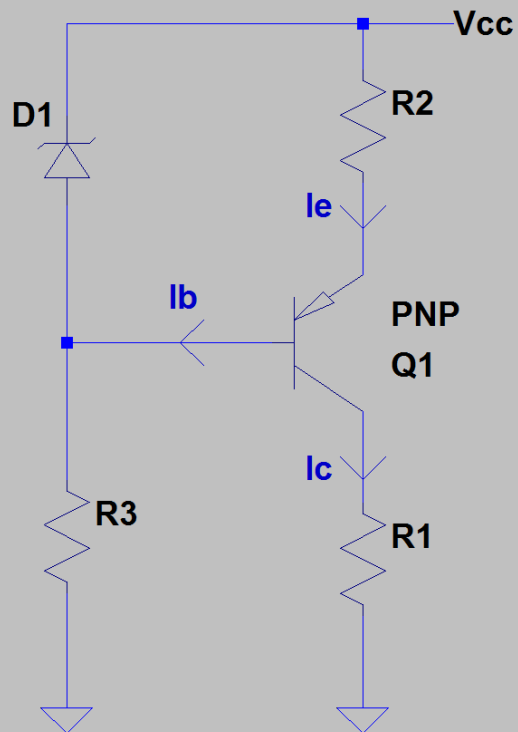


# Transmitter za Pt100

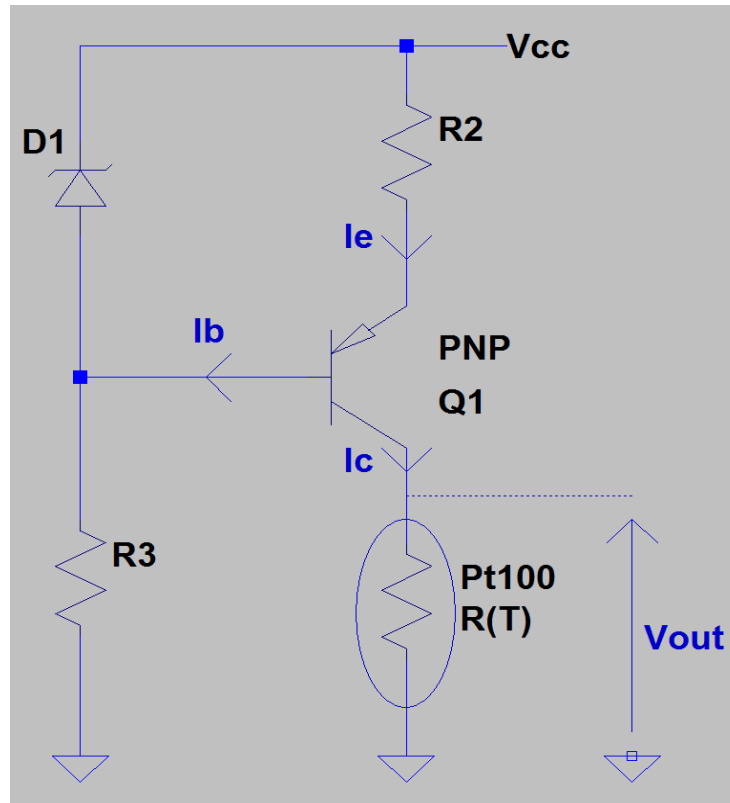

$$V_{out} = I_c \cdot R(T) \quad \text{pri čemu je } I_c = \text{const}$$

# Polarizacija tranzistora

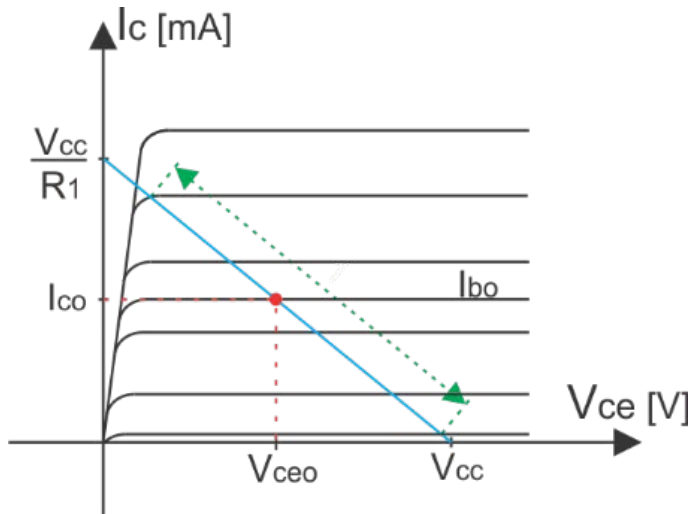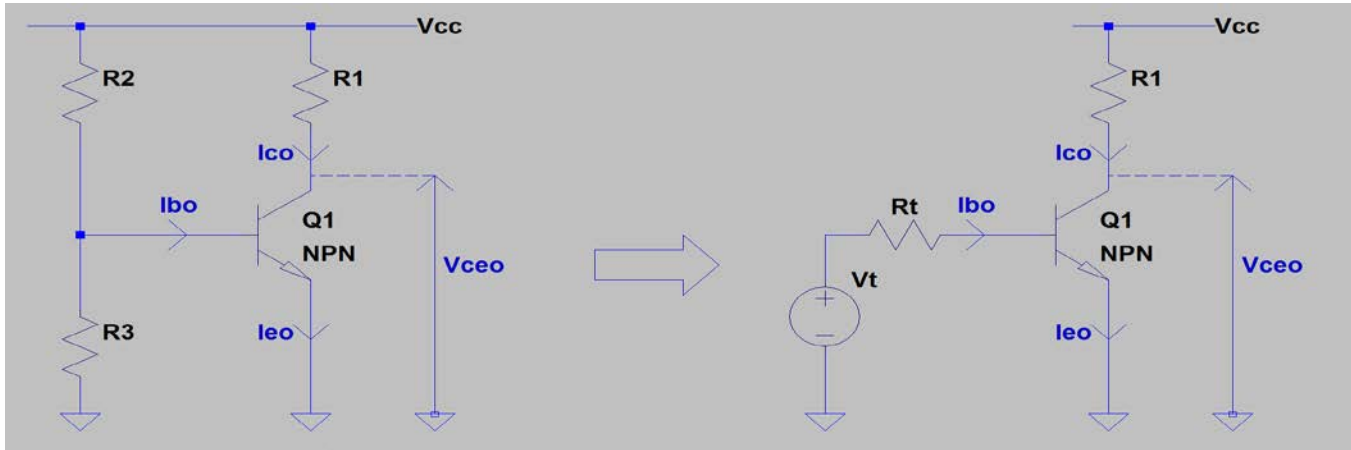



$$V_t = V_{cc} \cdot \frac{R_3}{R_2 + R_3} \quad i \quad R_t = \frac{R_2 \cdot R_3}{R_2 + R_3}$$

$$I_{bo} = \frac{V_t - V_{be}}{R_t}$$



$$I_{co} = h_{FE} \cdot I_{bo} = h_{FE} \cdot \frac{V_t - V_{be}}{R_t} \quad i$$

$$V_{ceo} = V_{cc} - R_1 \cdot I_{co}$$

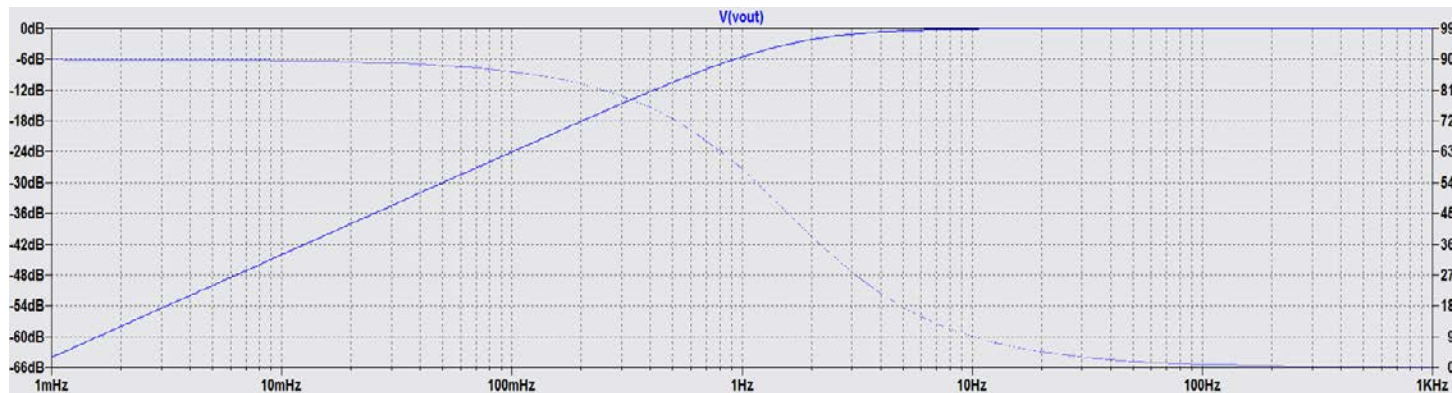
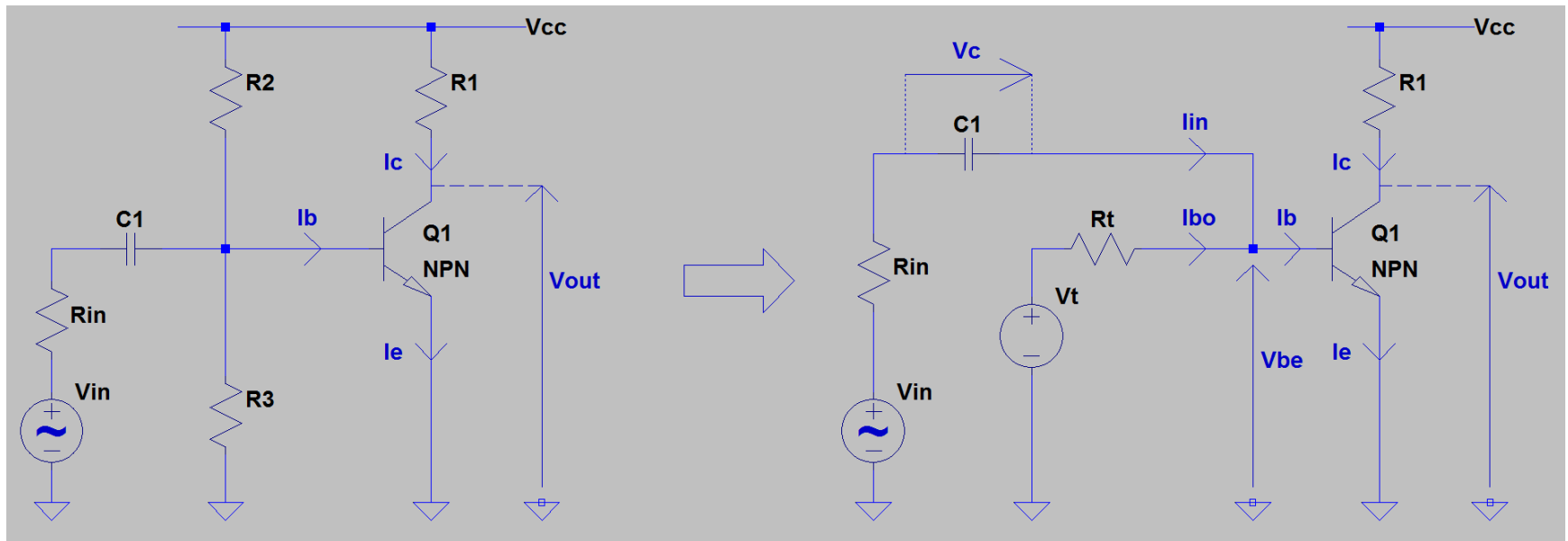
# Kapacitivna sprega za naizmenične signale



# Puš-pul pojačavač 1

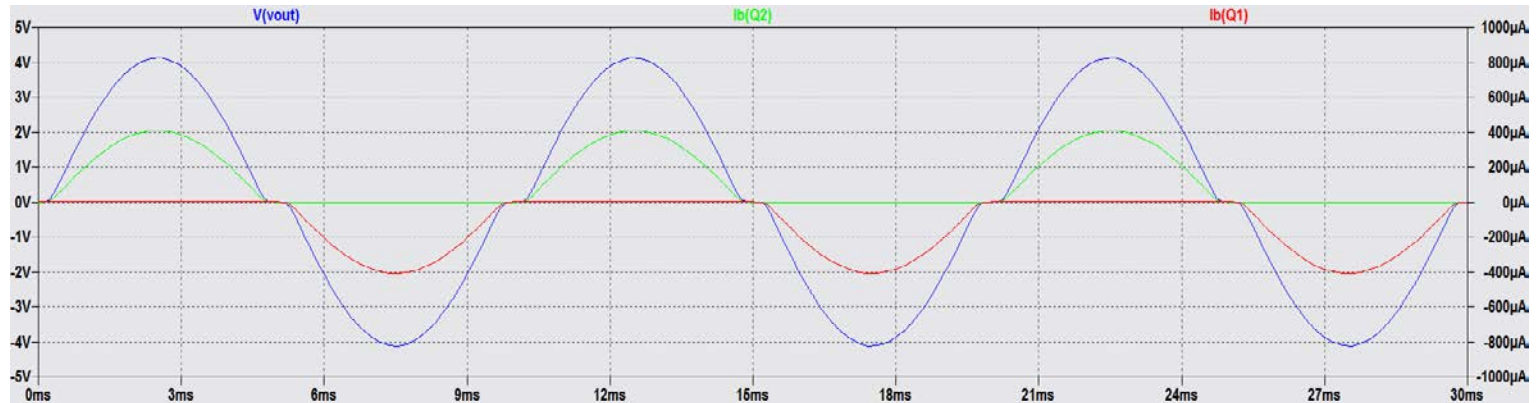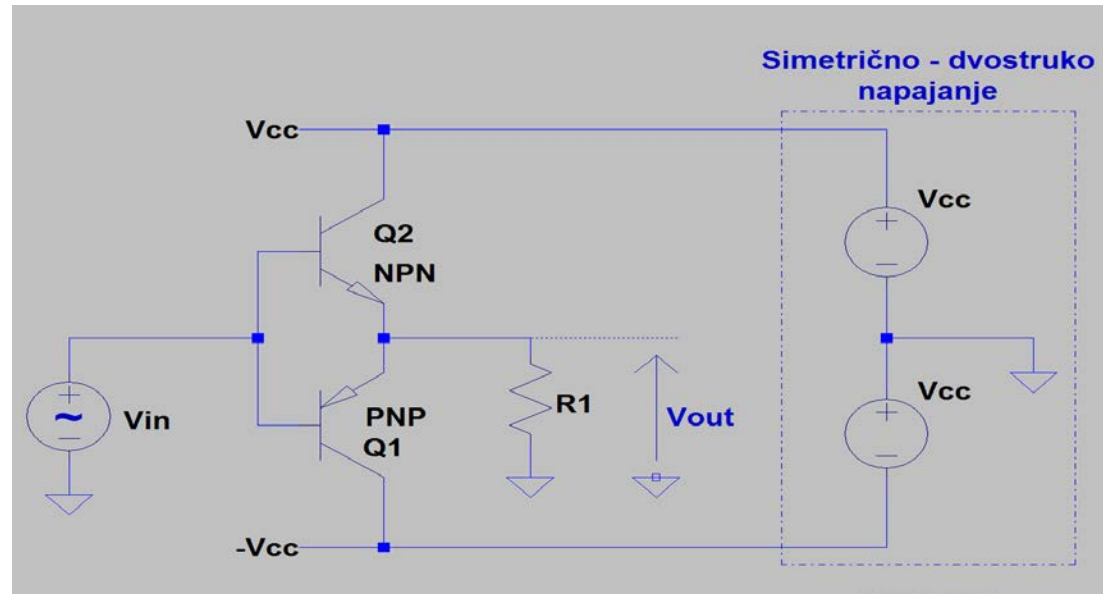


# Puš-pul pojačavač 2

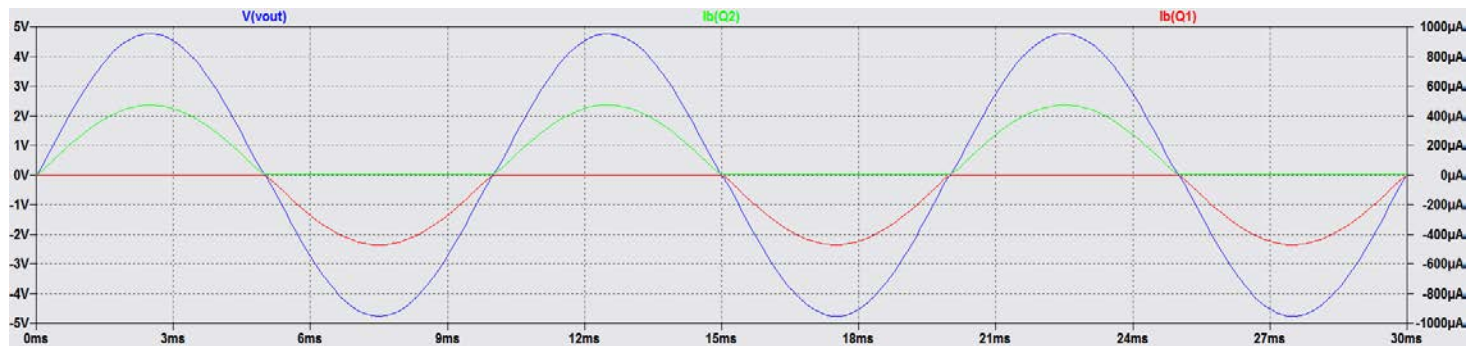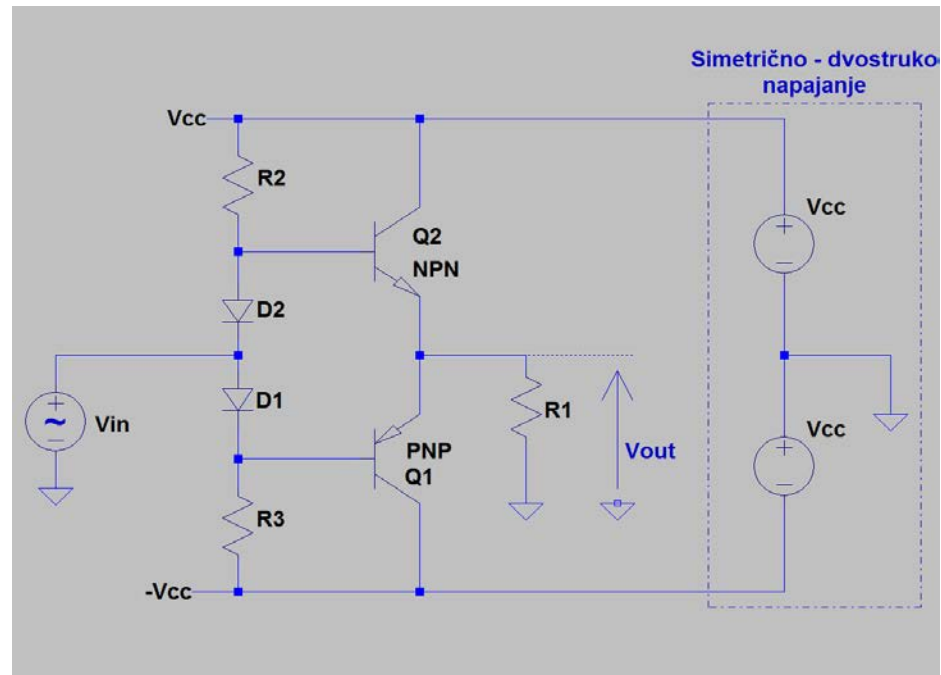




# NPN tranzistor kao prekidač

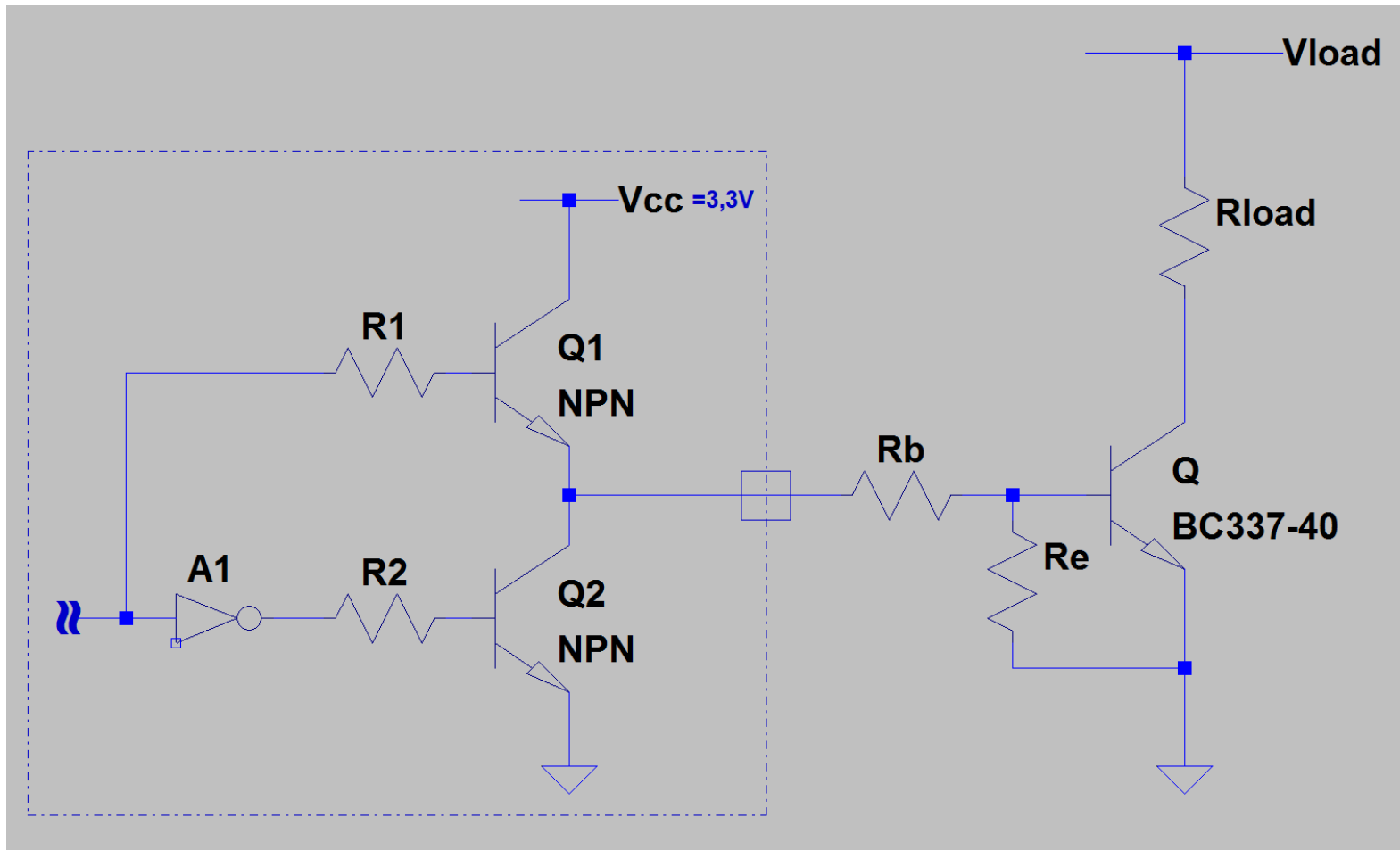

# PNP tranzistor kao prekidač

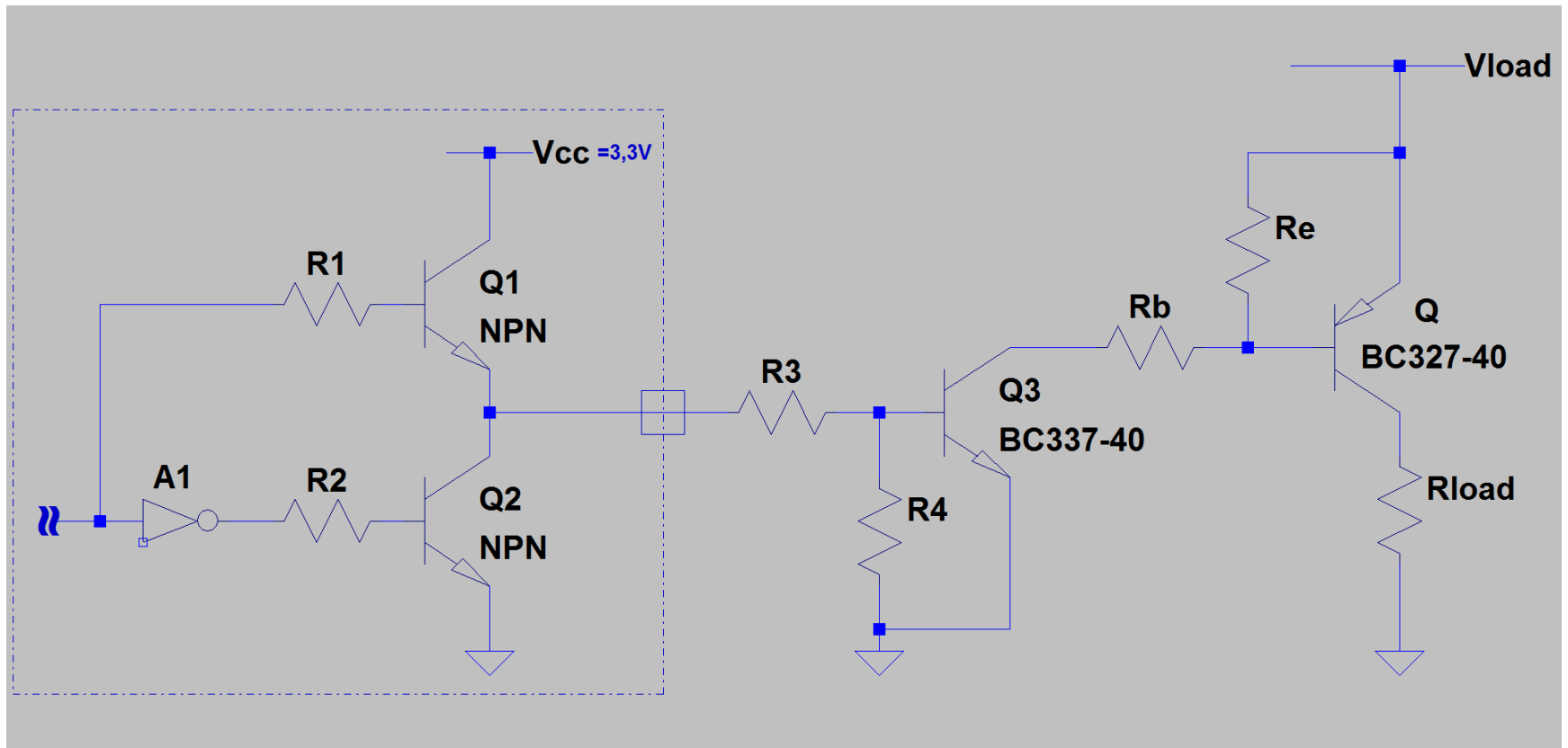

**Table 37-7. I/O pin characteristics.**

Symbol	Parameter	Condition		Min.	Typ.	Max.	Units
$I_{OH}^{(1)}$ / $I_{OL}^{(2)}$	I/O pin source/sink current			-20		20	mA
$V_{IH}$	High level input voltage	$V_{CC} = 2.7 - 3.6V$		2		$V_{CC}+0.3$	V
		$V_{CC} = 2.0 - 2.7V$		$0.7 \cdot V_{CC}$		$V_{CC}+0.3$	
		$V_{CC} = 1.6 - 2.0V$		$0.7 \cdot V_{CC}$		$V_{CC}+0.3$	
$V_{IL}$	Low level input voltage	$V_{CC} = 2.7 - 3.6V$		-0.3		$0.3 \cdot V_{CC}$	
		$V_{CC} = 2.0 - 2.7V$		-0.3		$0.3 \cdot V_{CC}$	
		$V_{CC} = 1.6 - 2.0V$		-0.3		$0.3 \cdot V_{CC}$	
$V_{OH}$	High level output voltage	$V_{CC} = 3.0 - 3.6V$	$I_{OH} = -2mA$	2.4	$0.94 \cdot V_{CC}$		
		$V_{CC} = 2.3 - 2.7V$	$I_{OH} = -1mA$	2.0	$0.96 \cdot V_{CC}$		
			$I_{OH} = -2mA$	1.7	$0.92 \cdot V_{CC}$		
		$V_{CC} = 3.3V$	$I_{OH} = -8mA$	2.6	2.9		
		$V_{CC} = 3.0V$	$I_{OH} = -6mA$	2.1	2.6		
		$V_{CC} = 1.8V$	$I_{OH} = -2mA$	1.4	1.6		
$V_{OL}$	Low level output voltage	$V_{CC} = 3.0 - 3.6V$	$I_{OL} = 2mA$		$0.05 \cdot V_{CC}$	0.4	
		$V_{CC} = 2.3 - 2.7V$	$I_{OL} = 1mA$		$0.03 \cdot V_{CC}$	0.4	
			$I_{OL} = 2mA$		$0.06 \cdot V_{CC}$	0.7	
		$V_{CC} = 3.3V$	$I_{OL} = 15mA$		0.4	0.76	
		$V_{CC} = 3.0V$	$I_{OL} = 10mA$		0.3	0.64	
		$V_{CC} = 1.8V$	$I_{OL} = 5mA$		0.3	0.46	
$I_{IN}$	Input leakage current				<0.001	0.1	$\mu A$
$R_P$	I/O pin Pull/Buss keeper resistor				25		k $\Omega$
$R_{RST}$	Reset pin pull-up resistor				25		
$t_r$	Pad rise time	No load			4.0		ns
			slew rate limitation		7.0		

- Notes:
1. The sum of all  $I_{OH}$  for PORTA, PORTC, PORTD, PORTE, PORTH, PORTJ, PORTK must for each port not exceed 200mA.  
The sum of all  $I_{OH}$  for PORTB must not exceed 100mA.  
The sum of all  $I_{OH}$  for PORTQ, PORTR and PDI must not exceed 100mA.
  2. The sum of all  $I_{OL}$  for PORTA, PORTC, PORTD, PORTE, PORTH, PORTJ, PORTK must for each port not exceed 200mA.  
The sum of all  $I_{OL}$  for PORTB must not exceed 100mA.  
The sum of all  $I_{OL}$  for PORTQ, PORTR and PDI must not exceed 100mA.

# Induktivni potrošači

Zaštitno kolo

